

Speed Regulation

$$SR = \frac{\omega_{m,nl} - \omega_{nA}}{\omega_{m,A}} \times 100\%$$

five types of Dc Motor

1. Separately Excited Dc Motor

2. Shunt \longrightarrow

3. permanent magnet \longrightarrow

4. Series \longrightarrow

5. Compound \longrightarrow

②


$E_A = K\phi\omega_m$ — (2) et. magnetomotive force

$T_{\text{ind}} = K\phi I_A$



$F = N_f I_f$ — (1)

from eq (1) and (2)

$I_f \propto \phi$

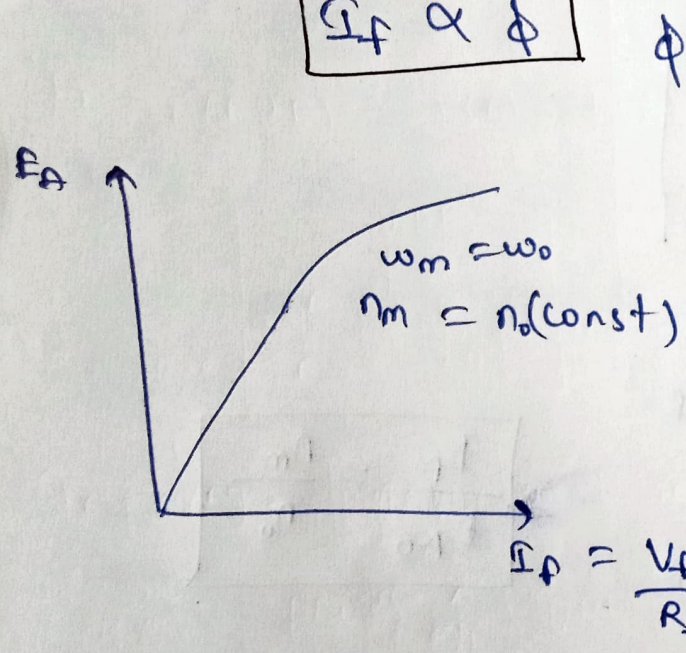


Separately Excited DC Motor

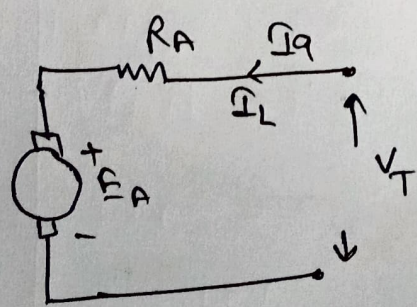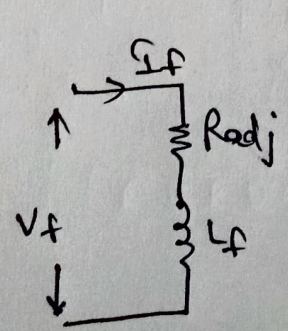

$I_f = \frac{V_f}{R_f}$

$V_T = E_A + I_A R_A$

$I_L = I_A$

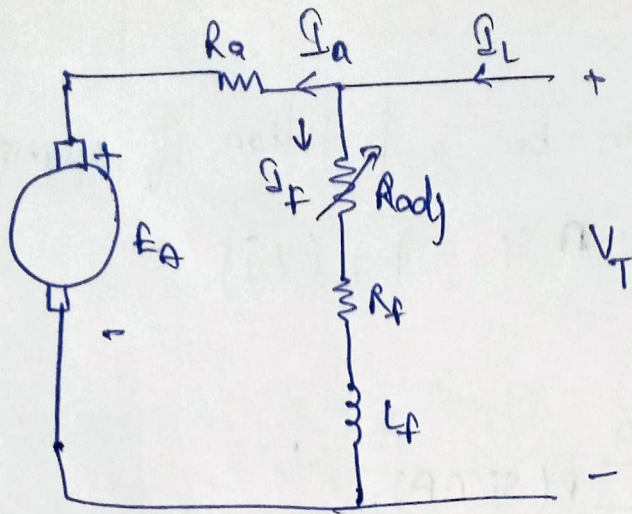

$$I_f = \frac{V_T}{R_f}$$

$$V_T = E_A + I_a R_a$$


$$I_L = I_a + I_f$$

As $V_T = E_A + I_a R_a$; $E_A = k\phi\omega_m$


$$\Rightarrow V_T = k\phi\omega_m + I_a R_a ; T_{ind} = k\phi I_a$$

$$V_T = k\phi\omega_m + \frac{T_{ind} \cdot R_a}{k\phi}$$

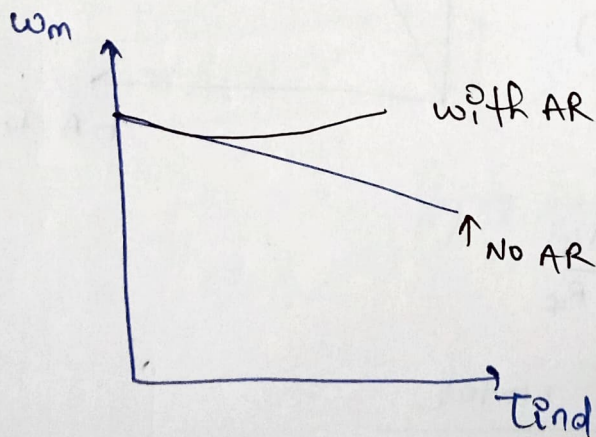
$$\Rightarrow \omega_m = \frac{V_T}{k\phi} - \frac{R_a}{(k\phi)^2} \cdot T_{ind}$$



$$\frac{E_A}{E_{A0}} = \frac{n_m}{n_0}$$

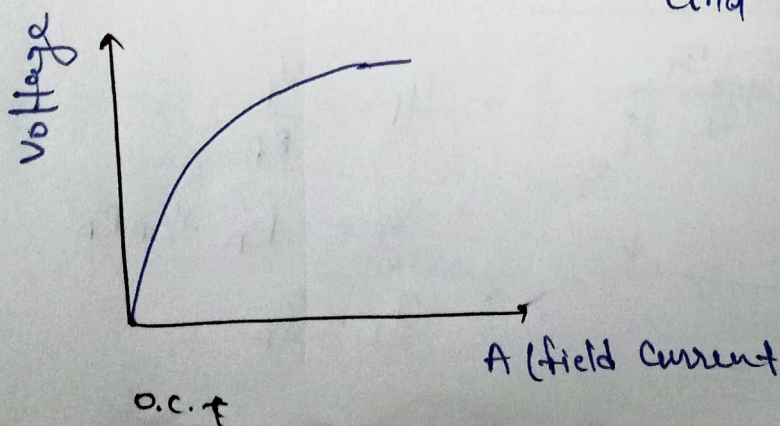

(4)

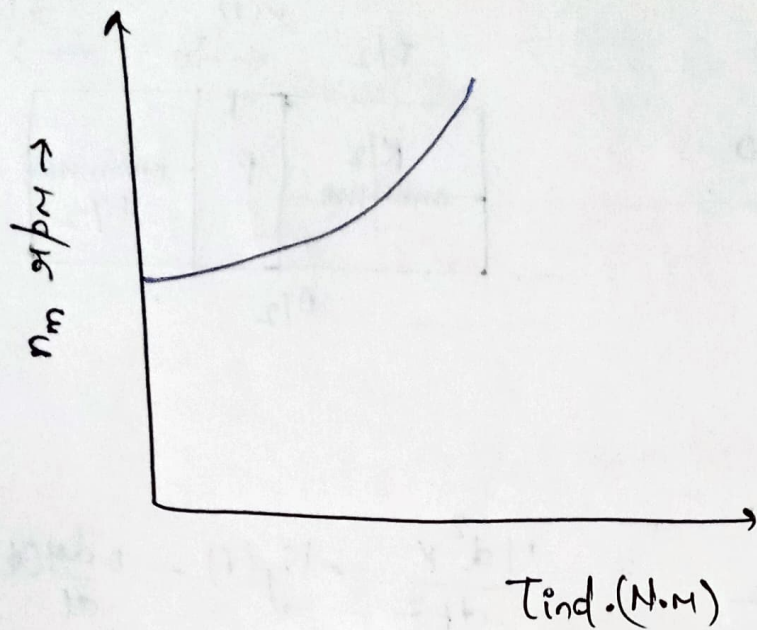

Torque speed characteristics of motor with AR.

Speed control of shunt DC motor


⑤

2 Most Common Method: -

1. field Resistance Adjustment
2. the terminal voltage applied to armature adjustment
3. connecting res. in series combination with the armature (rarely used).

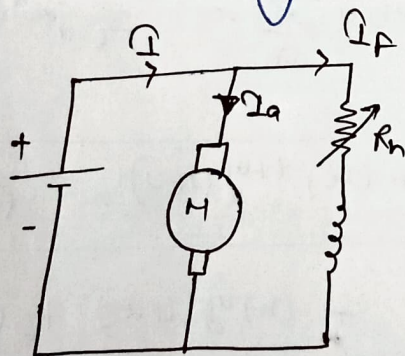1. Flux control Method: -

to control flux, A rheostat is added in series with the field winding.



$$I_f = \frac{V_T}{R_f}$$

$$I_f \propto \phi$$

As $R_h \uparrow$ $\phi \downarrow$ $N \uparrow$

$$E_A = K \phi \omega$$

$$T_{ind} = K \phi I_a$$

$$I_a = \frac{(V_T - E_A)}{R_a}$$


NOTE: - With decrement in flux of one %, 49% increment in armature current.

- increment in armature current dominant to decrement in flux that's why T_{ind} will also \uparrow .


As T_{ind} larger than T_{load} so speed will \uparrow .

⑥ Now. due to \uparrow in speed internal generated voltage $E_A \uparrow$ that cause to decrement in Armature current.

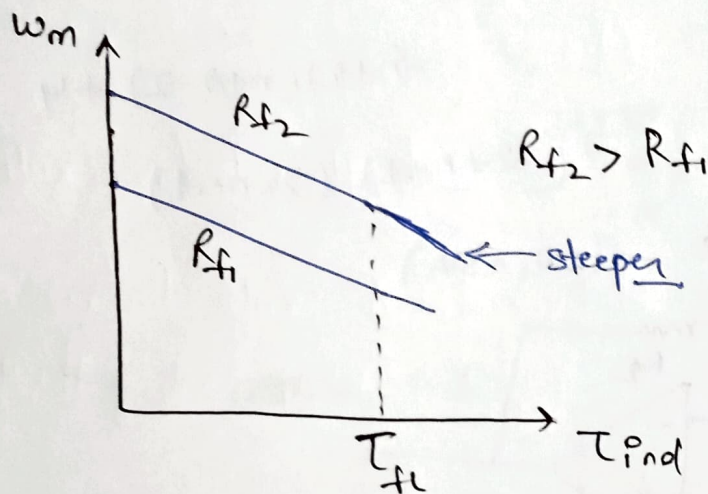As Armature current \downarrow Torque Induced \downarrow to become equal to T_{load} .



changing Armature Resistance:—

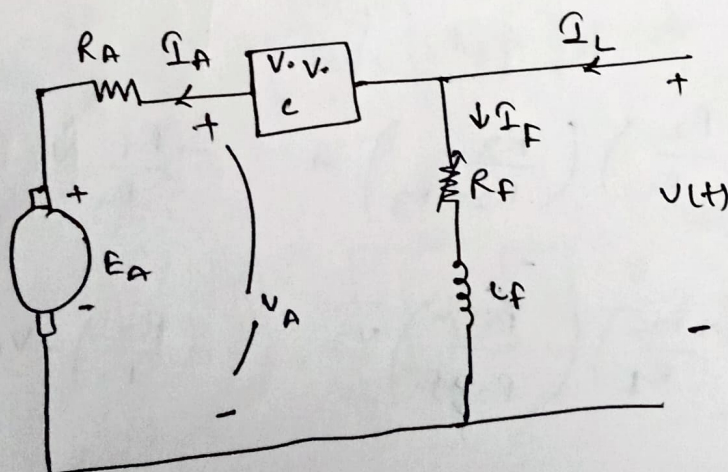

- The Motor should be in Separately excited for armature voltage control.

- If we \uparrow armature voltage V_A due to Arm. (7)
current also \uparrow


$$I_A = \frac{V_A - E_A}{R_A}; \quad T_{ind} = K\phi I_A$$

As $I_A \uparrow$ with \uparrow in V_A


due to ϕ_{res} $T_{ind} \uparrow > T_{load} \Rightarrow N \uparrow$ (Speed)

As speed $\uparrow \Rightarrow$ internal voltage $E_A \uparrow \Rightarrow I_A \downarrow \Rightarrow T_{ind} \downarrow$

$\therefore T_{ind} = T_{load}$

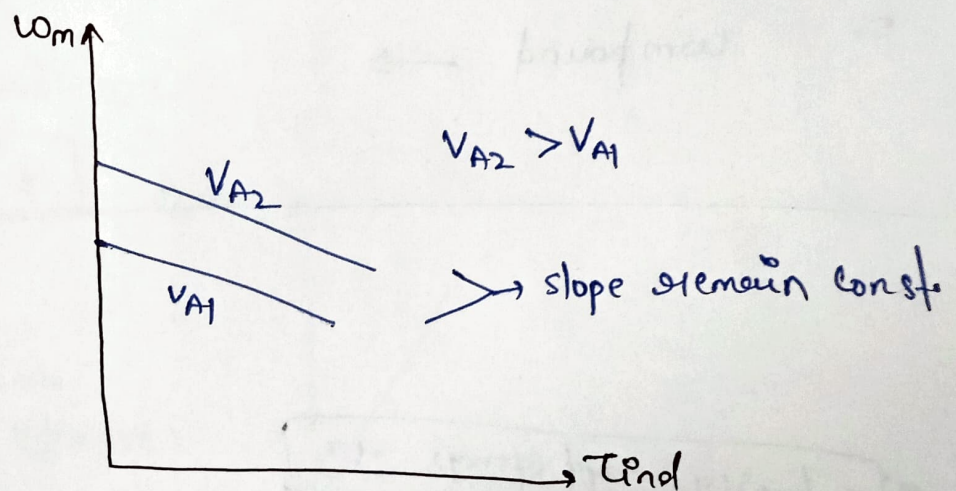


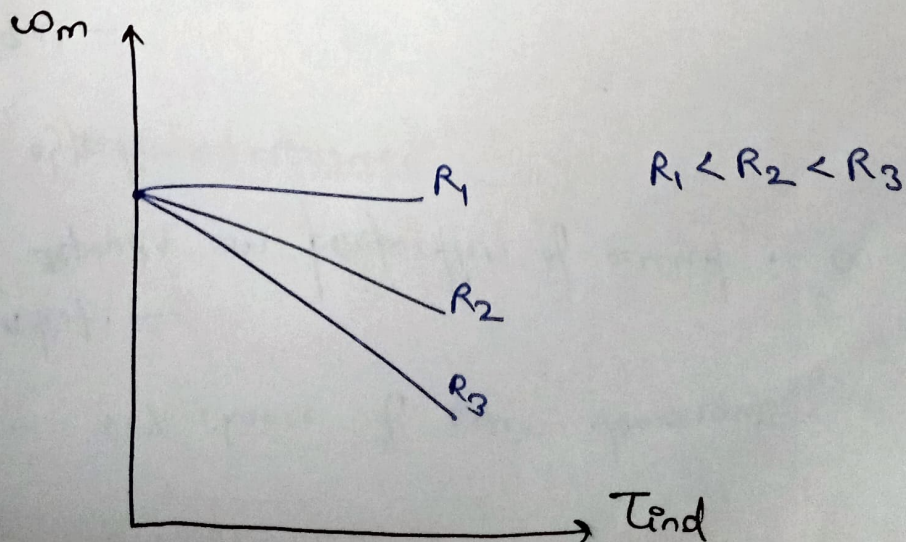
Inserting of resistance in series with Armature winding:-



⑧


Base Speed:—

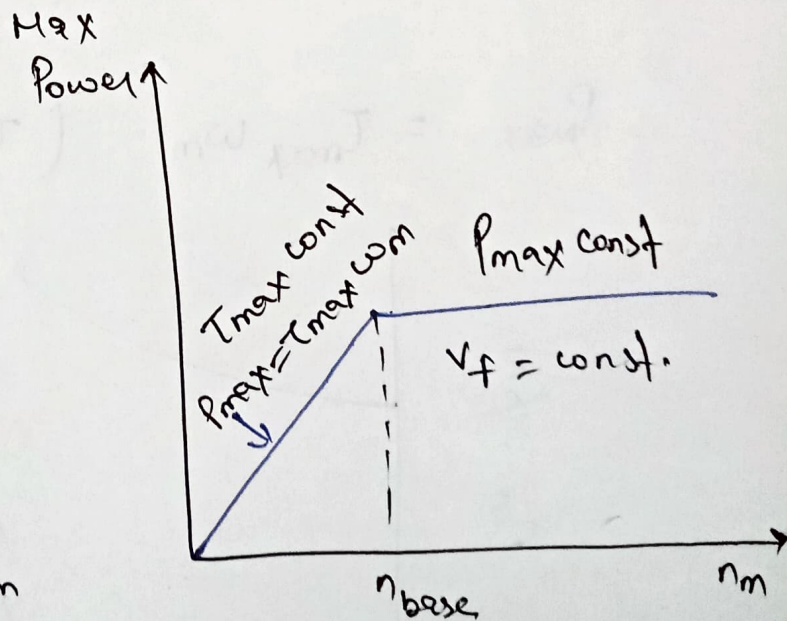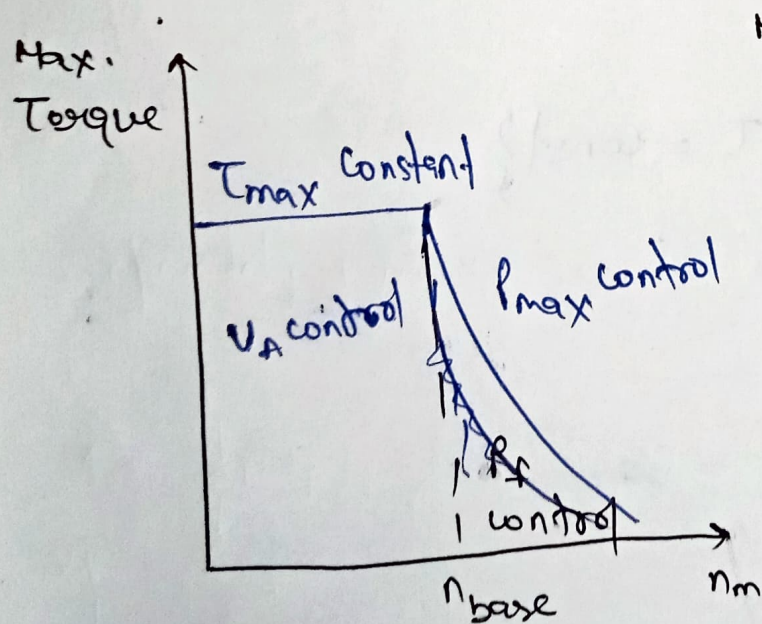If motor is operating at its rated terminal voltage, power, and field current, then it will be running at rated speed, also known as base speed.



$$\tau_{max} = K \phi I_a, max \quad \{ \phi = const \}$$
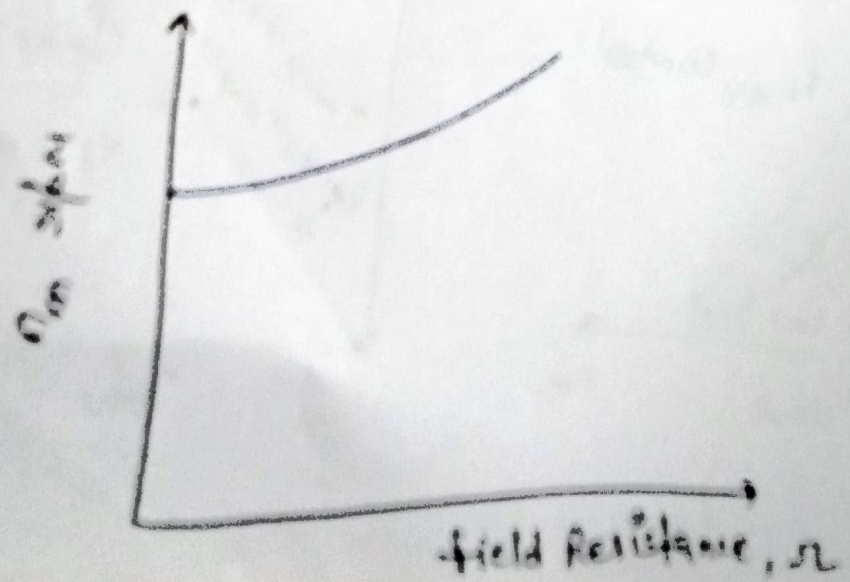
$$P_{max} = \tau_{max} \omega_m \quad \{ \tau = const \}$$



The Series DC Motor:—

(10)

$$V_T = E_A + I_A (R_A + R_S)$$

$$T_{ind} \propto \phi, \quad \phi \propto I_A \Rightarrow \phi = k I_A$$

$$T_{ind} \propto I_A^2$$

$$\Rightarrow \boxed{T_{ind} = k \phi I_A}$$

• Flux in this machine is directly proportional to its armature current (at least the metal saturates).

$$I_A = \sqrt{\frac{T_{ind}}{k c}}$$

$$\Rightarrow V_T = k \phi \omega_m + \sqrt{\frac{T_{ind}}{k c}} (R_A + R_S)$$

$$\text{As } I_A = \frac{\phi}{c}$$

$$T_{ind} = \frac{k}{c} \phi^2 \Rightarrow \phi = \sqrt{\frac{c}{k}} \sqrt{T_{ind}}$$


$$\omega_m = \frac{V_T}{\sqrt{k c}} - \frac{R_A + R_S}{k c}$$

if $T_{ind} = 0$ speed $= \infty$ (very high) \rightarrow practically.


• Never unload series motor.

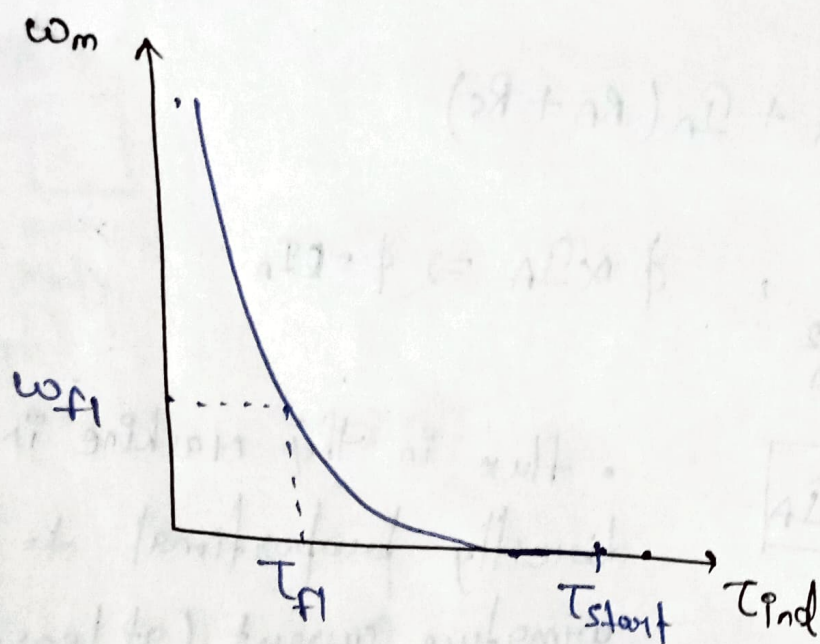(11)

with load there will be stray, mechanical and core losses so Torque will not be zero.



torque speed char. of a Series Dc motor.

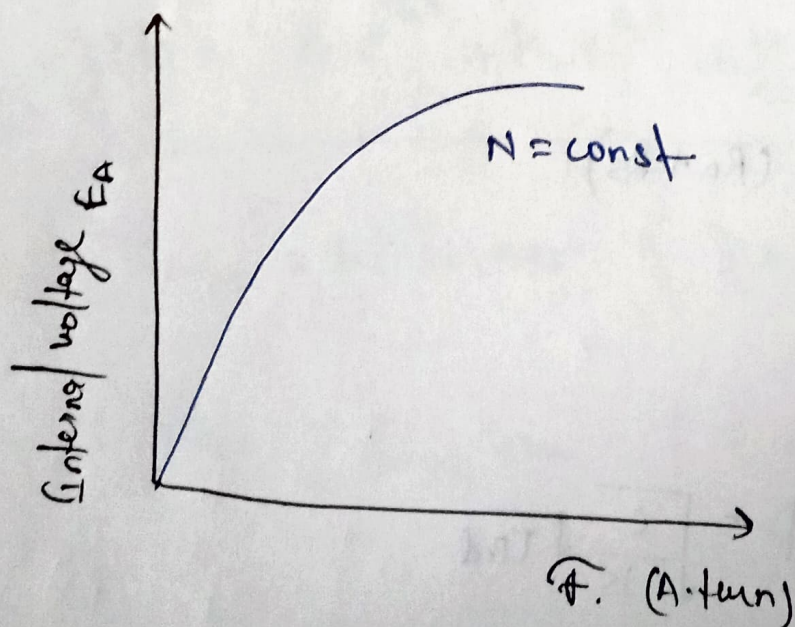

$$VR = \frac{V_{m1} - V_{f1}}{V_{f1}} \times 100\%$$